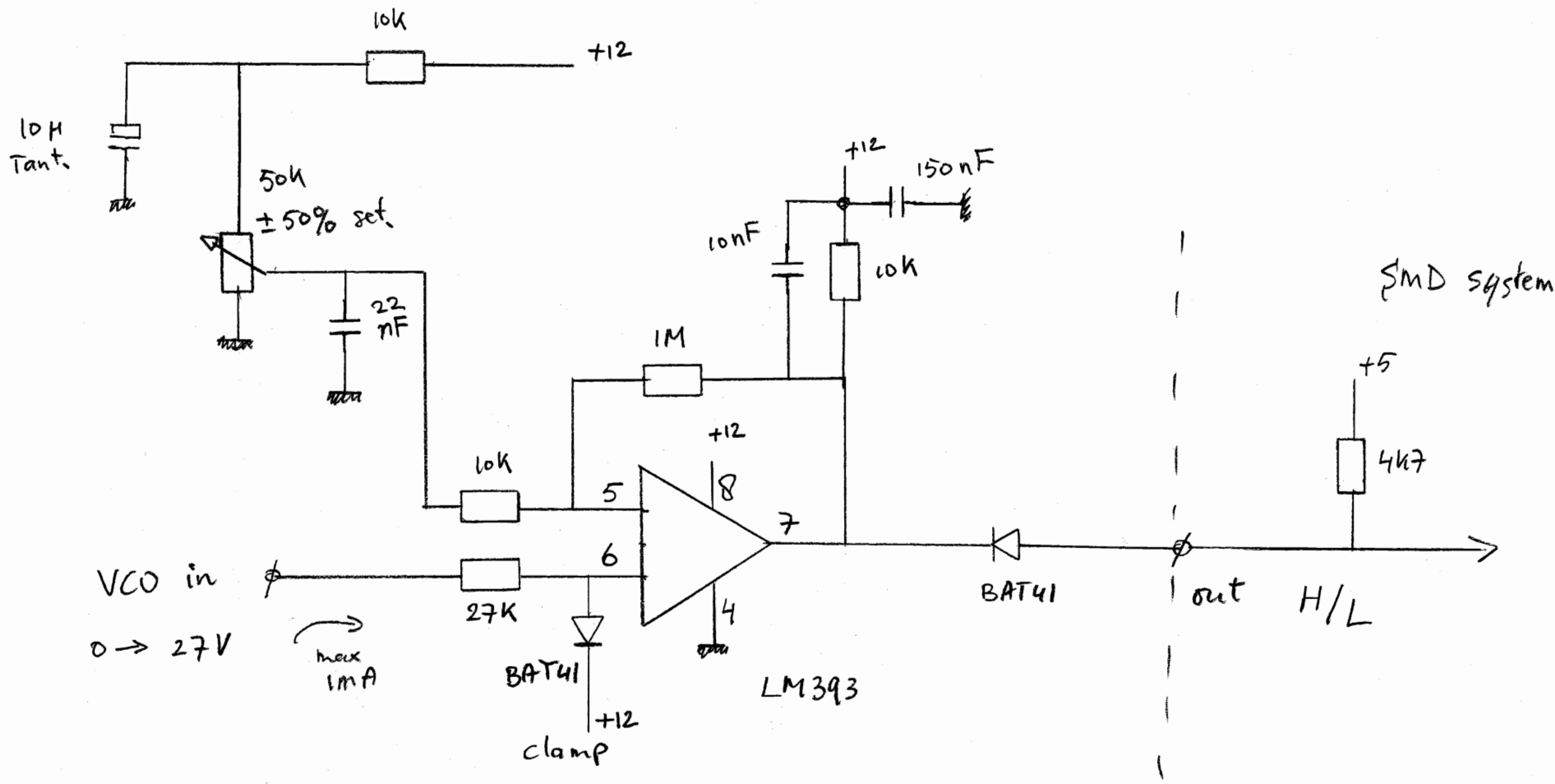


Sweeper counter control system

© PEI ABR
W. Geeraert

ALL IN SMD !!



VCO switch = $\pm 5V \hat{=} \pm 40-50MHz$

$U_{VCO} > 50MHz \rightarrow ECL \text{ on} \rightarrow \text{output} \hat{=} \text{low}$
above 5V


$U_{VCO} < 50MHz \rightarrow 74HC74 \text{ on} \rightarrow \text{output} \hat{=} \text{high}$
below 5V

auto input switch



sweeper counter

© PEIABR

CC displays !!

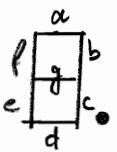

brightness
cobar

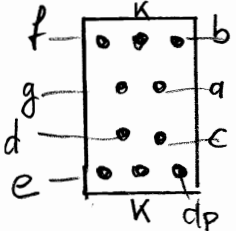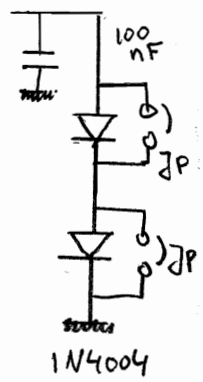


all outputs
SMD-C
position

HD 1077g
5 = green

4511
x4 →



all
330Ω

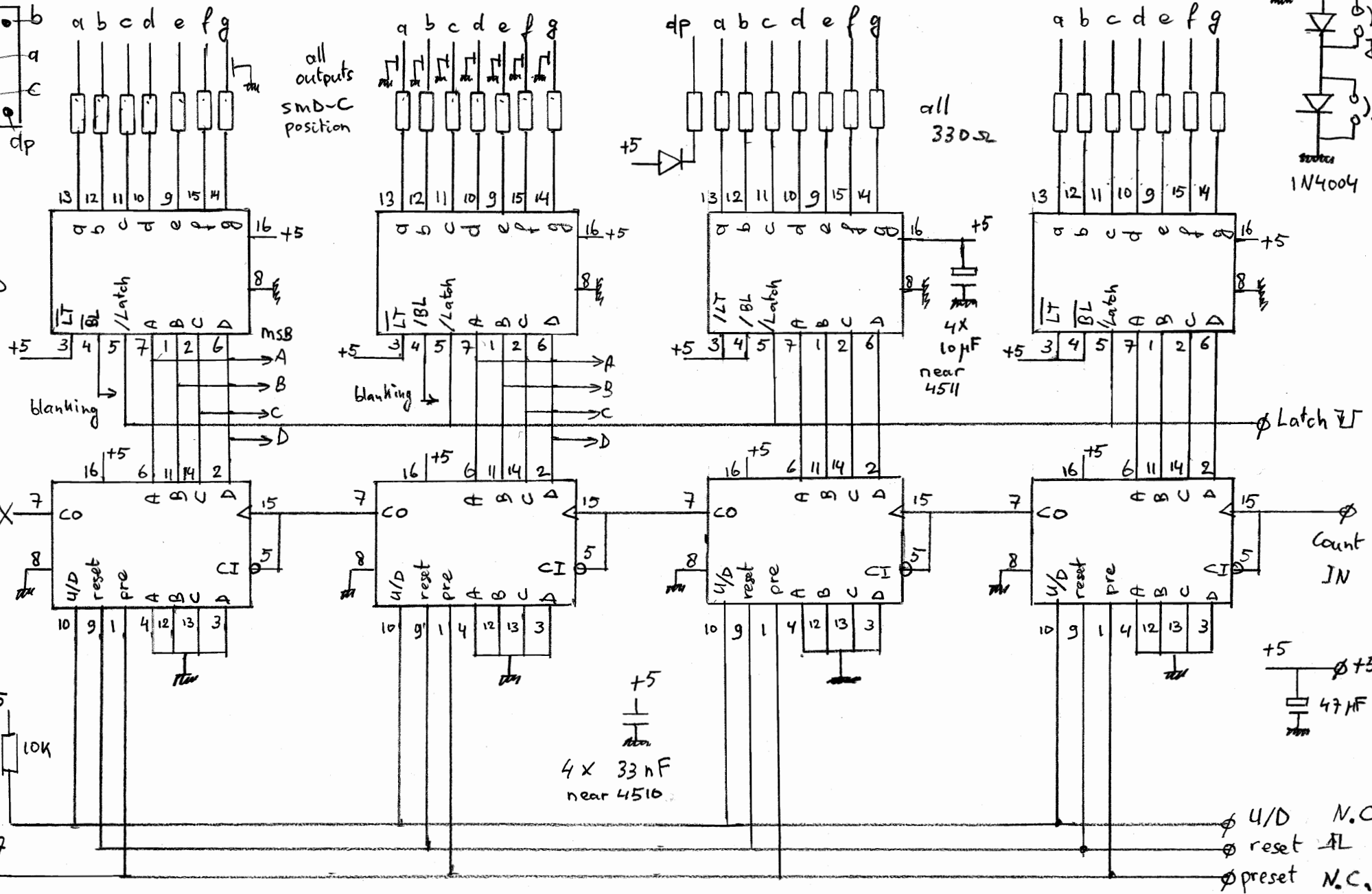

4510
x4 →


4 x 33 nF
near 4510

4 x 10 μF
near 4511





5V
47 μF

U/D N.C.
reset AL
preset N.C.


1st MSB
4510
↓
6-A
11-B
14-C
2-D

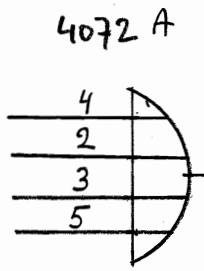


2nd MSB
4510
↓
6-A
11-B
14-C
2-D

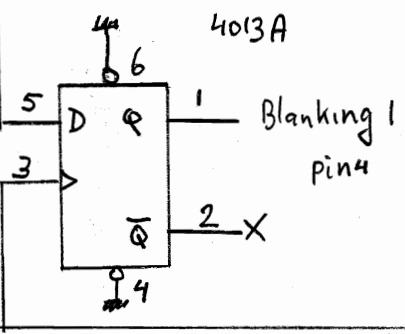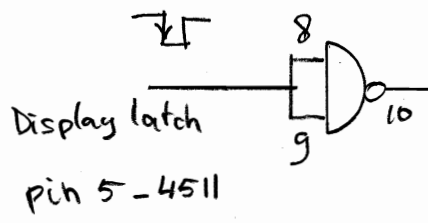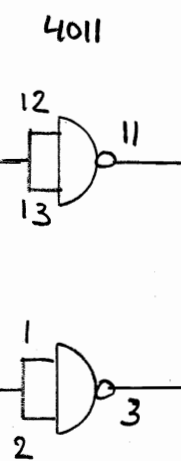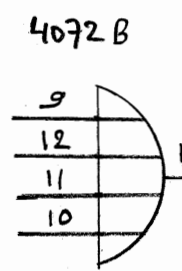

Blanking Latch

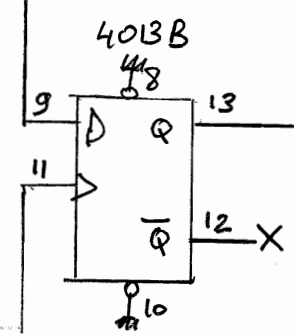

Blanking 2 pin 4

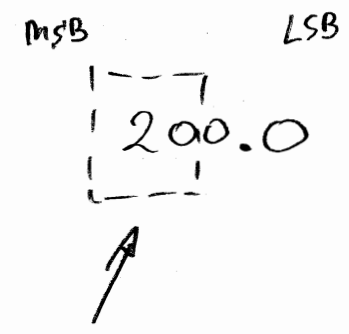

Ripple blanking
first 2 digits
sweeper counter

PEIABR

© W. Geeraert