







Two possible Z-transfer circuits

L-C version and with a toroid transformer

If needed NO common earth is possible with transformer

If not needed → short DC blocking 10nF

But: there shouldn't be any DC on the filter

Transformer Z = min. 4x circuit Z